

1. Berikan jawapan dalam perenambelasan bagi ungkapan perduaan berikut:

Give answer in hexadecimal for the following binary expression:

a)  $11101 + 101011$   
 $11101 + 101011$

(1 markah/mark)

b)  $1110 \times 110$   
 $1110 \times 110$

(1 markah/mark)

c)  $110011.10 - 110.11$   
 $110011.10 - 110.11$

(1 markah/mark)

a)

$$\begin{array}{r} 11101 \\ + 101011 \\ \hline 1001000_2 \end{array}$$

0100	1000
------	------

4            8

$48_{16}$

b)

$$\begin{array}{r} 1110 \\ \times 110 \\ \hline 0000 \\ 1110 \\ + 1110 \\ \hline 1010100_2 \end{array}$$

$$\begin{array}{r} 101 \quad 0100 \\ 5 \qquad \qquad 4 \end{array}$$

$54_{16}$

c)  $110011.10 - 110.11$

$$\begin{array}{r} 110011.10 \\ - 110.11 \\ \hline 101100.11 \end{array}$$

- A 1010
- B 1011
- C 1100

0010      1100      1100  
 2            C           C

$2CC_{16}$

Leith

2. Ringkaskan ungkapan berikut dengan menggunakan algebra Boolean;  
Simplify the following expressions using Boolean algebra:

$$BCDE + BC\overline{(DE)} + \overline{(BC)}DE$$

(4 markah/marks)

$$\begin{aligned} & BCDE + BC\overline{D}\overline{E} + \overline{B}\overline{C}DE \\ &= BCDE + BC\bar{D} + BC\bar{E} + \bar{B}DE + \bar{C}DE \\ &= DE(C + \bar{C}) + BC\bar{D} + BC\bar{E} + \bar{B}DE \\ &= DE(B + \bar{C}) + \dots \\ &= BDE + \bar{C}DE + BC\bar{D} + BC\bar{E} + \bar{B}DE \\ &= DE(B + \bar{B} + \bar{C}) + BC(\bar{D} + \bar{E}) \\ &= DE + BC(\bar{D} + \bar{E}) \end{aligned}$$

Leith

3. Reka satu litar logik gabungan yang mempunyai lima input (namakan sebagai A,B,C,D,E) dan satu output (namakan sebagai Y). Output akan menghasilkan keluaran logik-1 apabila majoriti input adalah logik-1 dan menghasilkan keluaran logik-0 apabila majoriti input adalah logik-0.

*Design a combinational logic with five-inputs (named as A, B, C, D, E) and one-output (named as Y). The output will produce a logic-1 output when the majority of its inputs are logic-1 and produce a logic-0 output when the majority of its inputs are logic-0.*

a) Tunjukkan jadual kebenaran untuk litar logik gabungan tersebut.

*Show the truth table for the combinational logic circuit.*

(4 markah/marks)

A B C D E  $\rightarrow$  Y

majority  $\geq 3$

					A=0	A=1	
	B	C	D	E	Y	Y	
0	0	0	0	0	0	0	16
1	0	0	0	1	0	0	17
2	0	0	1	0	0	0	18
3	0	0	1	1	0	1	19
4	0	1	0	0	0	0	20
5	0	1	0	1	0	1	21
6	0	1	1	0	0	1	22
7	0	1	1	1	1	1	23
8	1	0	0	0	0	0	24
9	1	0	0	1	0	1	25
10	1	0	1	0	0	1	26
11	1	0	1	1	1	1	27
12	1	1	0	0	0	1	28
13	1	1	0	1	1	1	29
14	1	1	1	0	1	1	30
15	1	1	1	1	1	1	31

Leith

b) Seterusnya, dapatkan Sum of minterm (SOM)

Then, get the Sum of Minterm (SOM)


(2 markah/marks)

$$F(A,B,C,D,E) = \sum_m (7, 11, 13, 14, 15, 19, 21, 22, 23, 25, 26, 27, 28, 29, 30, 31)$$

c) Berdasarkan SOM pada soalan 3b, lukiskan penyahkod 5 x 32 bagi mewakili jadual kebenaran tersebut.

Based on the SOM in question 3b, draw a 5x32 decoder to represent the truth table.


(2 markah/marks)

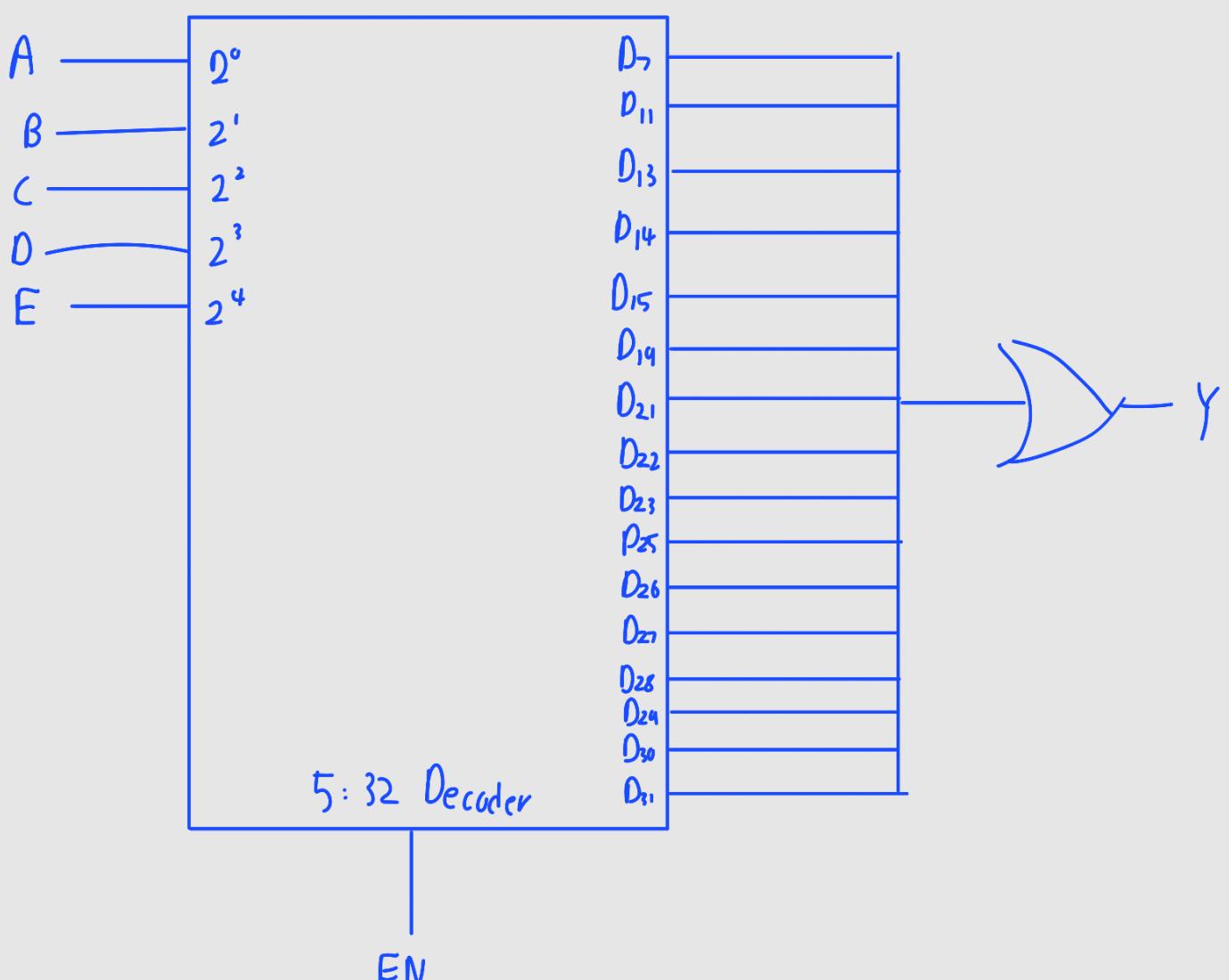

4)

Leith

A 4-bits Binary-coded Decimal (BCD) ( $A, B, C, D$ ) is used to light up a 7-segment display as in Figure 1. A combinational logic circuit is used to supply logic-1 to light up each segment in the 7-segment display.

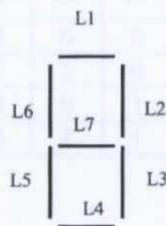

Rajah 1: paparan 7-semen  
Figure 1: 7-segments display

- a) Show the truth table for the combinational logic circuit with  $A, B, C$  and  $D$  as inputs and  $L_1$  to  $L_7$  as outputs. Assign the output as don't care if the input is not a BCD number.

(5 markah/marks)

Binary coded decimal

Valid : 0 - 9

Invalid: 10 - 15

 $L_1 - L_7$  $L_1$  : top segment $L_5$ : bottom-left segment $L_2$  : top-right segment $L_6$ : top-left segment $L_3$  : bottom-right segment  $L_7$ : Middle segment $L_4$ : bottom segment


$A$	$B$	$C$	$D$	$L_1$	$L_2$	$L_3$	$L_4$	$L_5$	$L_6$	$L_7$	
0	0	0	0	1	1	1	1	1	1	0	0
0	0	0	1	0	1	1	0	0	0	0	1
0	0	1	0	1	1	0	1	1	0	1	2
0	0	1	1	1	1	1	1	0	0	1	3
0	1	0	0	0	1	1	0	0	1	1	4
0	1	0	1	1	0	1	1	0	1	1	5
0	1	1	0	1	0	1	1	1	1	1	6
0	1	1	1	1	1	1	0	0	0	0	7
1	0	0	0	1	1	1	1	1	1	1	8
1	0	0	1	1	1	1	1	0	1	1	9
1	0	1	0	X	X	X	X	X	X	X	
1	0	1	1	X	X	X	X	X	X	X	
1	1	0	0	X	X	X	X	X	X	X	
1	1	0	1	X	X	X	X	X	X	X	
1	1	1	0	X	X	X	X	X	X	X	
1	1	1	1	X	X	X	X	X	X	X	

} Invalid BCD


Use Karnaugh map to get the simplified equation for each segments (L1-L7) in the 7-segment display.

Leith


(7 markah/marks)

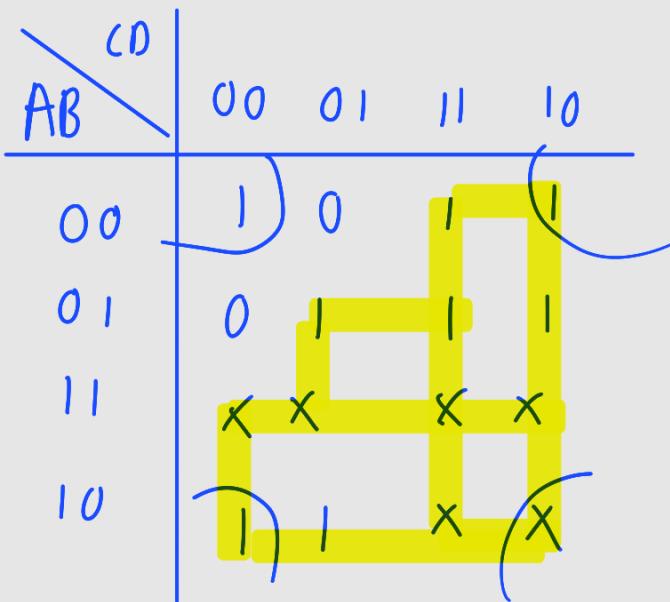


$$L1 = B'D' + C + A + BD$$

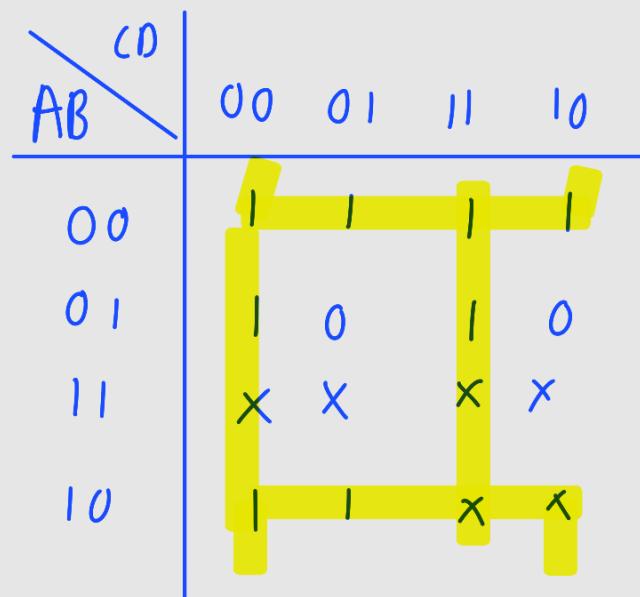


$$L2 = B' + C'D' + CD$$

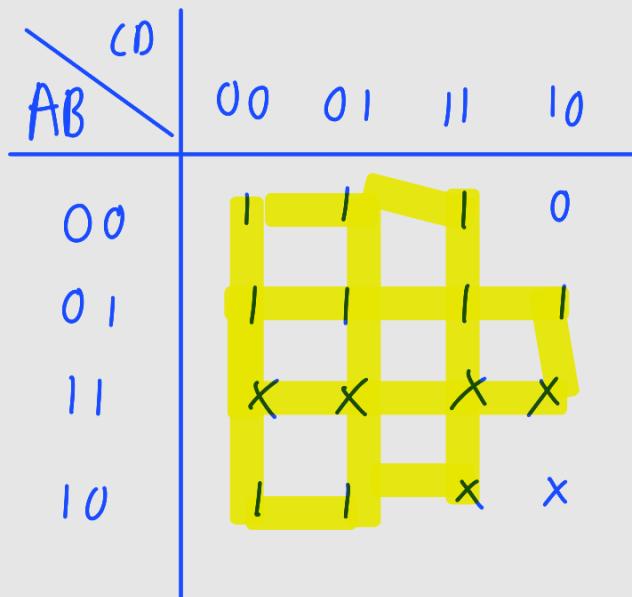


$$L3 = B + C' + D$$

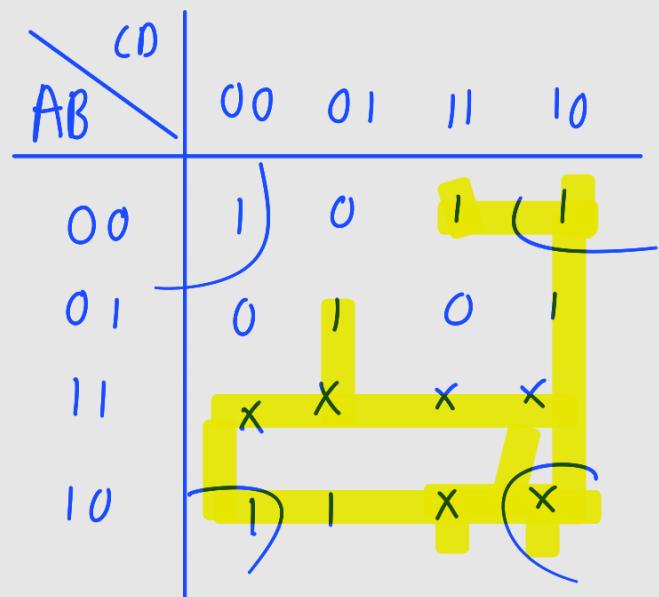


$$L4 = B'D' + B'C + BC'D + CD' + A$$

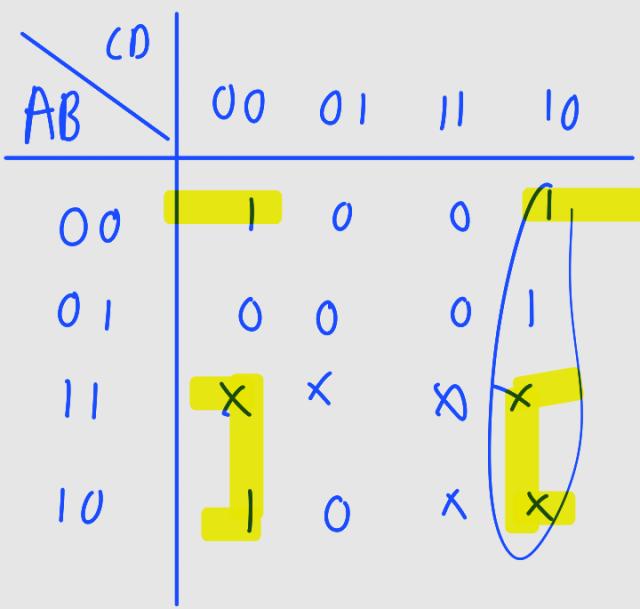

$$L_5: A'D' + A'B'D' + CD'$$

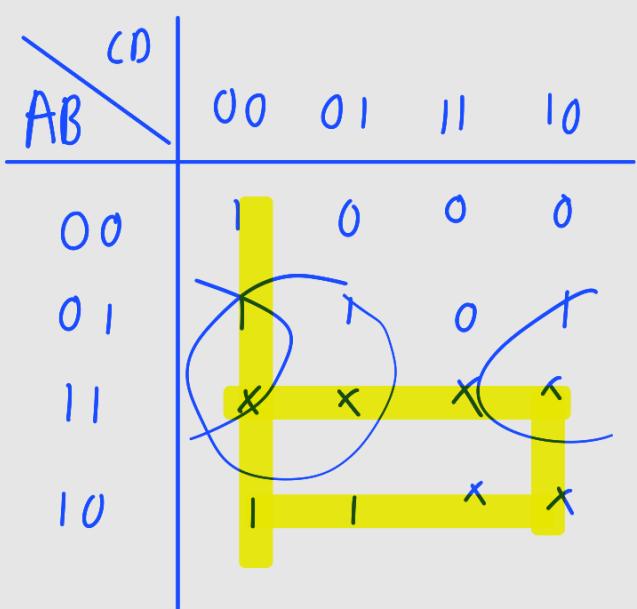

$$L_6: C'D' + BD' + BC' + A$$

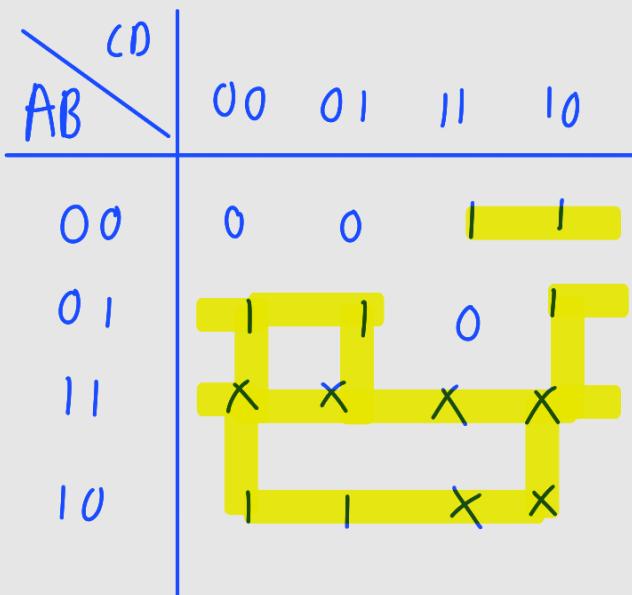

$$L_7: A'B'C + A + BC' + BD'$$

c)

Given only **THREE** types of logic gates which are OR gate, NOT gate and Exclusive-OR gate, build the combinational logic circuit for segment L1, L2 and L3.

Leith

(3 markah/marks)

$$L_1 = \bar{B}\bar{D} + C + A + BD$$


$$L_2 = \bar{B} + \bar{C}\bar{D} + CD$$

$$L_3 = B + \bar{C} + D$$

$$XOR = X\bar{Y} + \bar{X}Y$$

$$XNOR = \bar{X}\bar{Y} + XY \leftarrow \text{pattern match}$$


$\rightarrow$   $\rightarrow$

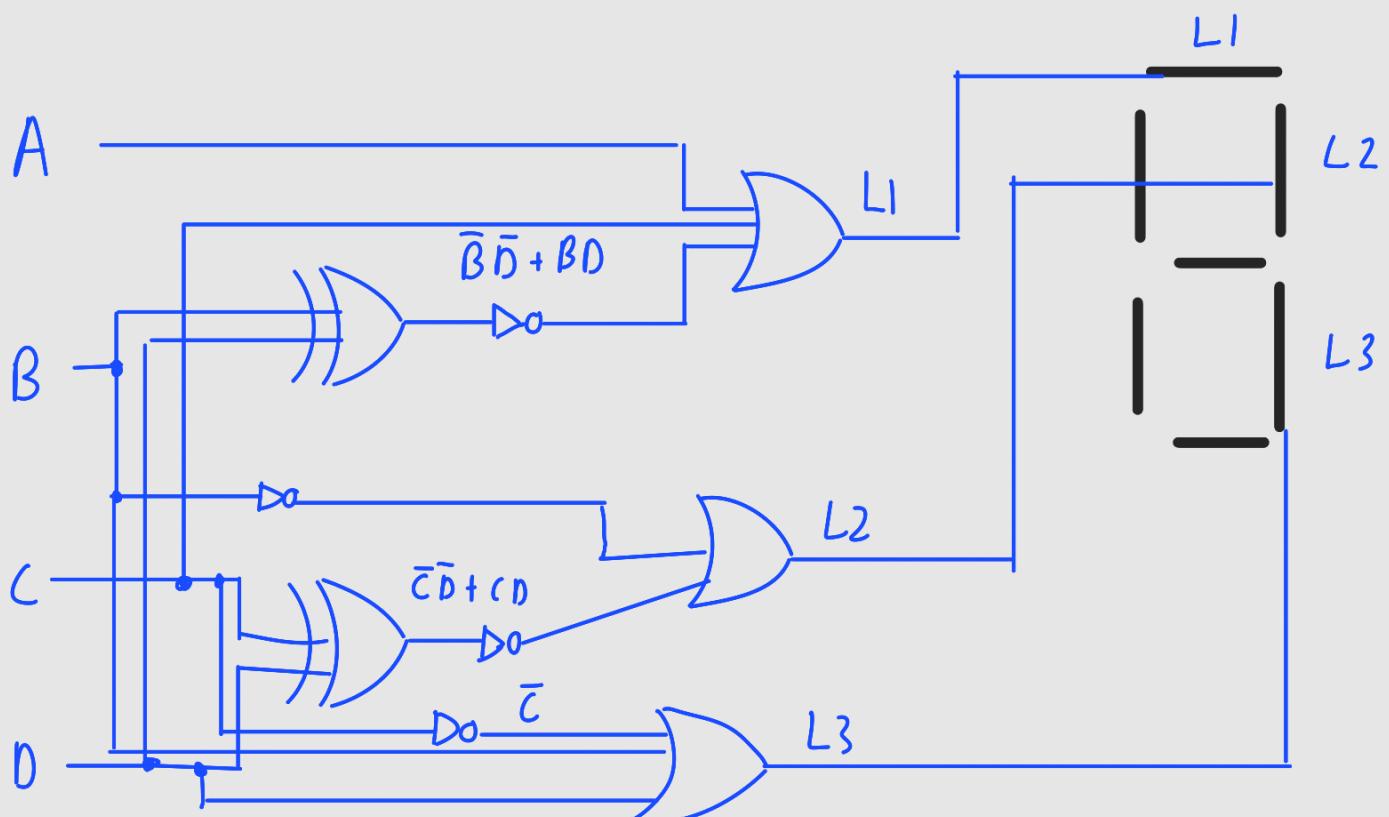

5)

By using a 4-bit adder as shown in Figure 2, determine the output  $\Sigma$  based on the given input as in the following table:

$X_1$	$X_2$	$X_3$	$X_4$	$Y_1$	$Y_2$	$Y_3$	$Y_4$	$\Sigma_1$	$\Sigma_2$	$\Sigma_3$	$\Sigma_4$	$\Sigma_5$
1	0	0	1	1	0	0	0	0	1	0	1	0
0	1	0	1	1	0	1	1	1	1	1	0	1
0	1	0	0	1	1	0	0	1	0	1	0	6
1	1	0	1	1	1	1	0	0	1	0	0	1

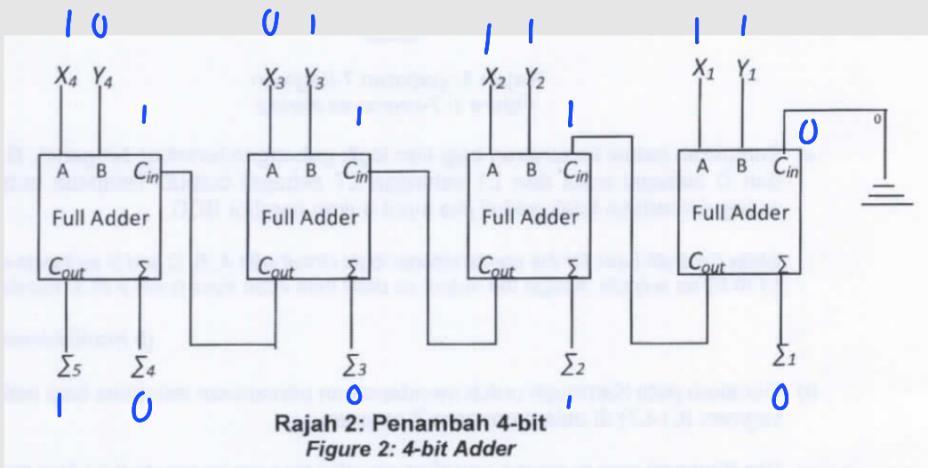

← right to left

A	B	Cin	Sum (S)	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Based on the state table as in Table 1, answer the following questions.

Leith

Keadaan Semasa Current State			Keadaan Berikut Next State		
A	B	C	A*	B*	C*
0	0	0	x	x	x
0	0	1	1	1	1
0	1	0	1	1	0
0	1	1	x	x	x
1	0	0	x	x	x
1	0	1	0	1	0
1	1	0	0	0	1
1	1	1	1	0	1

Jadual 1: Jadual keadaan  
Table 1: State table

a)

Show the maps for JK flip flops and get the JK flip-flop equation for  $J_A$ ,  $K_A$ ,  $J_B$ ,  $K_B$ ,  $J_C$  and  $K_C$ .

(4 markah/marks)

INPUT		OUTPUT	
Qn	Q(n+1)	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

A	B	C	$A^+$	$B^+$	$C^+$	$J_A$	$K_A$	$J_B$	$K_B$	$J_C$	$K_C$
0	0	0	x	x	x	x	x	x	x	x	x
0	0	1	1	1	1	1	x	1	x	x	0
0	1	0	1	1	0	1	x	x	0	0	x
0	1	1	x	x	x	x	x	x	x	x	x
1	0	0	x	x	x	y	x	x	x	x	x
1	0	1	0	1	0	x	1	x	0	x	1
1	1	0	0	0	1	x	1	x	1	1	x
1	1	1	1	0	1	x	0	x	1	x	0

$\overline{A}$	$\overline{B}C$	00	01	11	10
0	x	1	x	1	
1	x	x	x	x	x

$\overline{A}$	$\overline{B}C$	00	01	11	10
0	x	x	x	x	x
1	x	1	1	0	1

$$\overline{J_A} = 1$$

$$K_A = B' + C'$$

A \ BC	00	01	11	10
0	X	I	X	X
1	X	X	X	X

$$J_B = 1$$

A \ BC	00	01	11	10
0	X	X	X	0
1	X	X	X	I

$$J_C = A$$

A \ BC	00	01	11	10
0	X	X	X	0
1	X	0	I	I

$$K_B = AB$$

A \ BC	00	01	11	10
0	X	0	X	X
1	X	I	0	X

$$K_C = AB'$$

b)

Based on the JK flip-flop equation from question 6a, get the next state for the states that are not in the cycle (i.e 000; 011; 100).

Keadaan Semasa Current State			JK Flip Flop						Keadaan Berikut Next State		
A	B	C	J <sub>A</sub>	K <sub>A</sub>	J <sub>B</sub>	K <sub>B</sub>	J <sub>C</sub>	K <sub>C</sub>	A*	B*	C*
0	0	0	I	I	I	0	0	0	I	I	0
0	1	1	I	0	I	0	0	0	I	I	I
1	0	0	I	I	I	0	I	I	0	I	I

(4 markah/marks)

$$J_A = I$$

$$K_A = \bar{B} + \bar{C}$$

$$J_B = I$$

$$K_B = AB$$

$$J_C = A$$


$$K_C = A\bar{B}$$

J	K	Q <sub>n+1</sub>
0	0	Q <sub>n</sub>
0	1	0
1	0	1
1	1	Q <sub>n'</sub>

c)

Show the full state diagram.

(2 markah/marks)

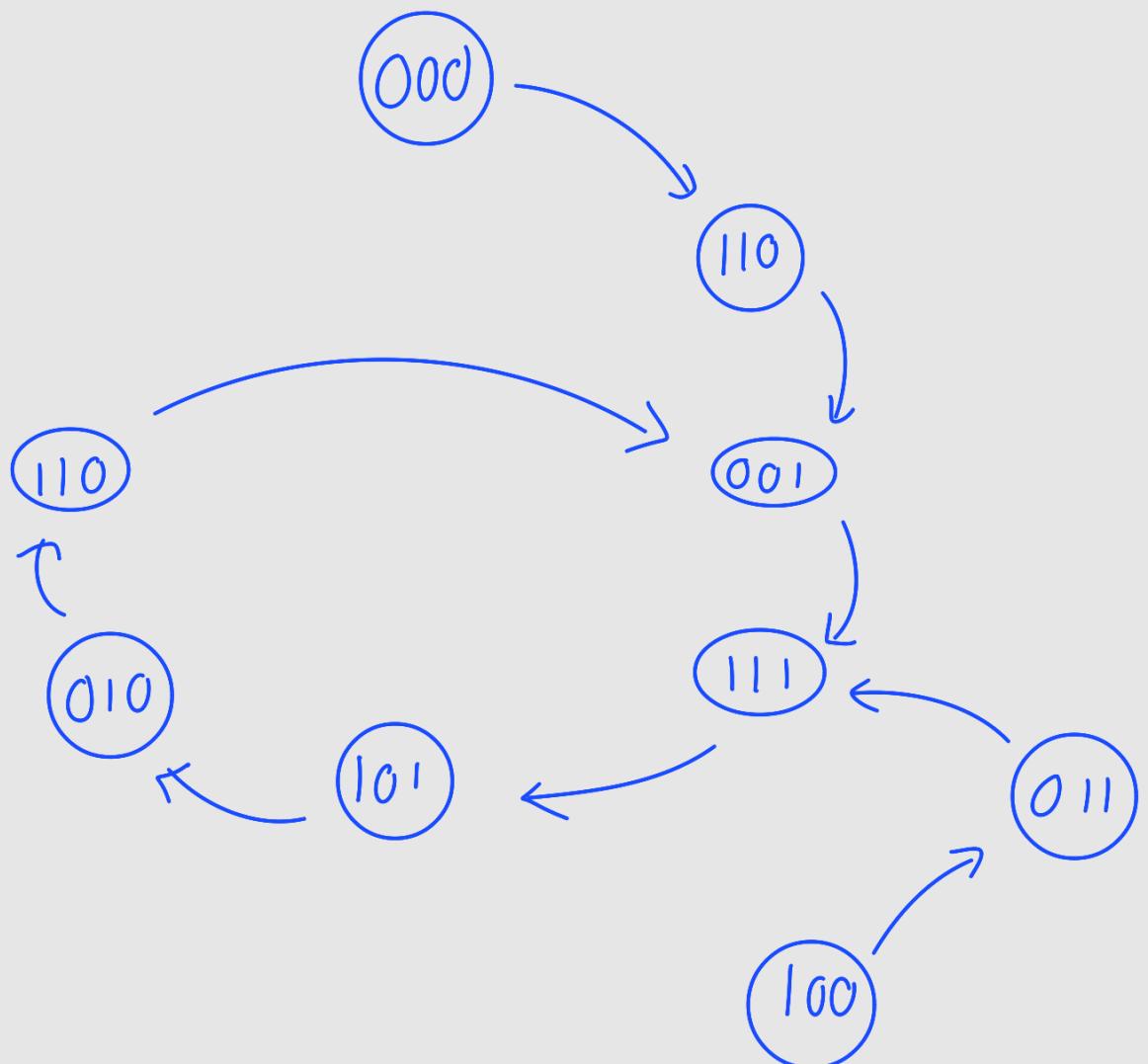

If a register starts with 101001111000 state, what is their state after:

Leith

7)

a) Putar-Kanan dengan 2 detik kitaran?

Rotate-Right with 2 clock pulse?

(2 markah/marks)

--	--	--	--	--	--	--	--	--	--	--	--	--	--	--

ori

1	0	1	0	0	1	1	1	1	1	0	0	0
---	---	---	---	---	---	---	---	---	---	---	---	---

①

0	1	0	1	0	0	1	1	1	1	0	0
---	---	---	---	---	---	---	---	---	---	---	---

②

0	0	1	0	1	0	0	1	1	1	1	0
---	---	---	---	---	---	---	---	---	---	---	---

free mark

b)

By using the current state from question 7a, Rotate-Left with 5 clock pulse.

(3 markah/marks)

ori:

0	0	1	0	1	0	0	1	1	1	1	0
---	---	---	---	---	---	---	---	---	---	---	---

0	1	0	1	0	0	1	1	1	1	1	0	0
---	---	---	---	---	---	---	---	---	---	---	---	---

1	0	1	0	0	1	1	1	1	1	0	0	0
---	---	---	---	---	---	---	---	---	---	---	---	---

0	1	0	0	1	1	1	1	1	0	0	0	1
---	---	---	---	---	---	---	---	---	---	---	---	---

1	0	0	1	1	1	1	1	0	0	0	1	0
---	---	---	---	---	---	---	---	---	---	---	---	---

0	0	1	1	1	1	1	0	0	0	1	0	1
---	---	---	---	---	---	---	---	---	---	---	---	---

free mark