

Geith

1)

Find the minterm (Σm) for the following equation:

a) $F(A,B,C)=A+BC$

$F(A,B,C)=A+BC$

? list everything under
the sun

(2 markah/marks)

$$A \rightarrow 10^4, 10^5, 110^6, 111^7$$

$$BC \rightarrow \textcircled{011}^3, 111^7$$

$$F(A,B,C) = \sum m(3,4,5,6,7)$$

b) $F(A,B,C,D)=(A+C')(B+C+D')$

$F(A,B,C,D)=(A+C')(B+C+D')$

$$= \bar{A}C + \bar{B}\bar{C}D \quad (3 \text{ markah/marks})$$

$$\bar{A}C \rightarrow 0010_2, 0011_3, 0110_6, 0111_7$$

$$\bar{B}\bar{C}D \rightarrow 0001_1, 1001_9$$

$$F(A,B,C,D) = \sum m(1,2,3,6,7,9)$$

Draw the following logical gates using NAND gates only.

a) $F(A, B, C) = B + AC$


$$F(A, B, C) = B + AC$$

b)


D_o

(3 markah/marks)
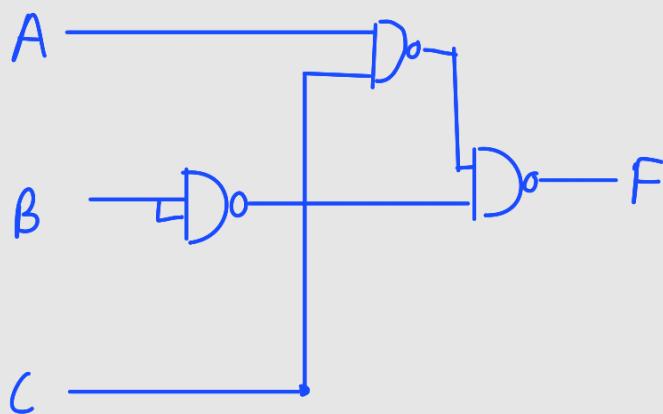
$$\begin{aligned} \bar{F} &= \overline{\overline{B + AC}} \\ &= \overline{\overline{B} \cdot \overline{AC}} \end{aligned}$$



b)

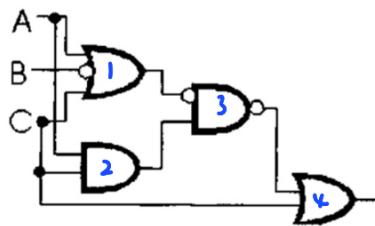


(5 markah/marks)

$$G1 = A + \bar{B} + C \quad G3 = \overline{(A + \bar{B} + C) AC}$$

$$G2 = AC \quad G4 = \overline{(A + \bar{B} + C) AC} + C$$

Simplify G4
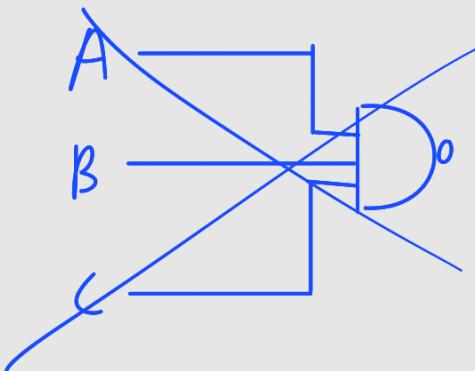
$$\begin{aligned} &\overline{(A + \bar{B} + C) AC} + C \\ &= \overline{A + \bar{B} + C} + \overline{AC} + C \\ &= A + \bar{B} + C + \bar{A} + \bar{C} + C \\ &= 1 \leftarrow \text{constant true} \end{aligned}$$



V_{CC} — F



Leith

3) If the original 5-bit register value is 11001, what is its value after:

a) Putar kanan empat kali.

Rotate right four times.

(1 markah/mark)

ori

1	1	0	0	1
---	---	---	---	---

--	--	--	--	--

1	0	0	1	1
0	0	1	1	1
0	1	1	1	0
1	1	1	0	0

free mark

b) Logical shift left three times.

(1 markah/mark)

original
sabahan

1	1	0	0	1
---	---	---	---	---

LSL (logical shift left)
just delete it

1	0	0	1	0
0	0	1	0	0
0	1	0	0	0


c) Logical shift right two times.

(1 markah/mark)

original
sabahan

1	1	0	0	1
---	---	---	---	---

0	1	1	0	0
0	0	1	1	0

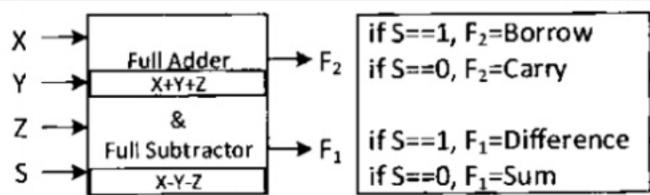

Rajah 1: Penambah Penuh dan Penolak Penuh
Figure 1: Full Adder and Full Subtractor

4)

Full adder and full subtractor can be built in a single combinational logic circuit by using an input signal to select between the two function. The input and output of the combinational logic circuit is shown in Figure 1. If S equals to 1, the circuit works as a full subtractor and if S equals to 0, the circuit works as a full adder.

- a) Tunjukkan jadual kebenaran bagi litar logik bergabungan.

Show the truth table for the combinational logic circuit.

(4 markah/marks)

			$S=0$	$S=1$		
A	B	C	F_1	F_2	F_1	F_2
0	0	0	0	0	0	0
0	0	1	1	0	1	1
0	1	0	1	0	1	0
0	1	1	1	1	0	1
1	0	0	0	0	1	0
1	0	1	0	1	0	1
1	1	0	0	0	0	1
1	1	1	1	1	1	1

Inputs			Outputs	
A	B	C_{in}	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Inputs			Outputs	
A	B	$Borrow_{in}$	Diff	$Borrow$
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

b)

Obtain the simplified Sum of Product (SOP) of F_2 and F_1 by using Karnaugh Map.

Leith

(4 markah/marks)

SA \ BC	00	01	11	10
00	0	1	0	1
01	1	0	1	0
11	1	0	1	0
10	0	1	0	1

$$F_1 = AB'C' + A'B'C + ABC + A'BC'$$

SA \ BC	00	01	11	10
00	0	0	1	0
01	0	1	1	1
11	0	0	1	0
10	0	1	1	1

$$F_2 = BC + S'AC + S'AB + SA'C + SA'B$$

c)

Based on the SOP in question 1b, draw the combinational logic circuit by using only 3 Exclusive-OR gate, 2 AND gate and 2 OR gate.

(4 markah/marks)

$$F_1 = AB'C' + A'B'C + ABC + A'BC'$$

$$= C(A'B' + AB) + C'(A'B + AB') \quad \text{Let } K = A'B + AB'$$

$$= C K' + C'K \quad K' = A'B' + AB$$


$$F_2 = BC + S'AC + S'AB + SA'C + SA'B$$

$$= C(S'A + SA') + BC(S'A + A'S) + BC \quad \text{Let } X = AS' + A'S$$

$$= CX + BX + BC$$

$$= X(B + C) + BC$$


Leith

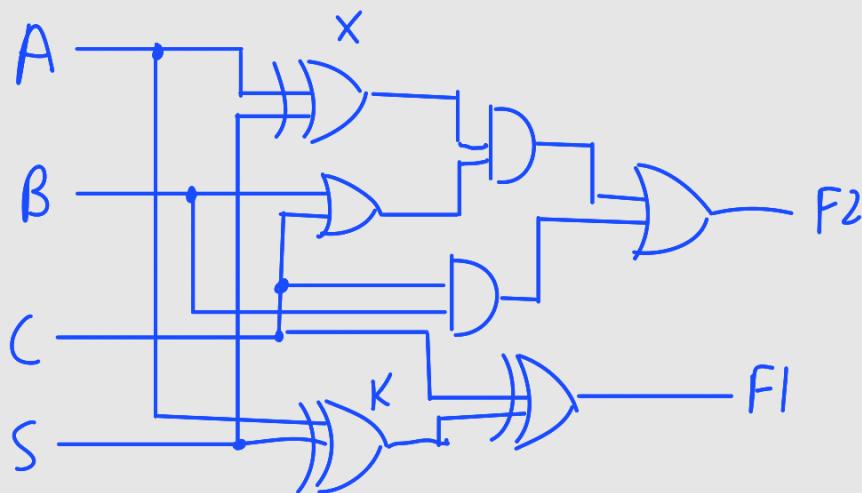

3 XOR

2 AND

2 OR

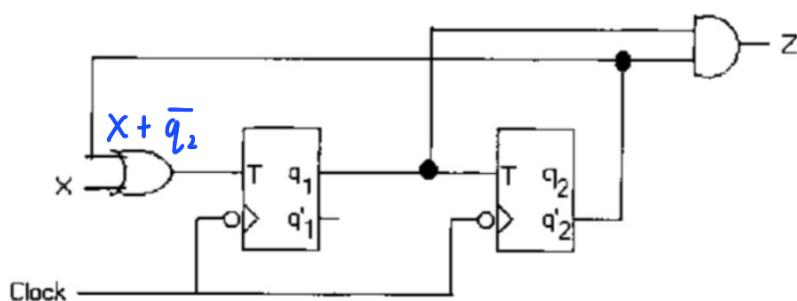

Rajah 2: Litar logik jujukan
Figure 2: Sequential circuit

5

Based on Figure 2, answer the following questions:

- a) Berikan persamaan untuk T_1 , T_2 dan Z .

Give the equation for T_1 , T_2 and Z .

(3 markah/marks)

$$T_1 = X + \bar{q}_2$$

$$T_2 = q_1$$

$$Z = q_1 \cdot \bar{q}_2$$

b) Fill up the following state table based on equation obtained in a

Leith

10

Jadual 1: Jadual keadaan.

Table 1: State table.

x	q1	q2	q1+	q2+	T1	T2	z
0	0	0	1	0	1	0	0
0	0	1	0	1	0	0	0
0	1	0	0	1	1	1	1
0	1	1	1	0	0	1	0
1	0	0	1	0	1	0	0
1	0	1	1	1	1	0	0
1	1	0	0	1	1	1	1
1	1	1	0	0	1	1	0

$$T1 = X + \bar{q}_2$$

$$T2 = q_1$$

$$Z = q_1 \cdot \bar{q}_2$$

CLK	T	Q _n	Q _{n+1}
↓	0	0	0
↓	0	1	1
↓	1	0	1
↓	1	1	0


(5 markah/marks)

- c) Berikan gambar rajah keadaan untuk jadual keadaan yang didapati dari (b).
Give the state diagram for state table obtained in (b).

q1 q2 x/z

x	q1	q2	q1+	q2+	z
0	0	0	1	0	0
0	0	1	0	1	0
0	1	0	0	1	1
0	1	1	1	0	0
1	0	0	1	0	0
1	0	1	1	1	0
1	1	0	0	1	1
1	1	1	0	0	0

(2 marka)

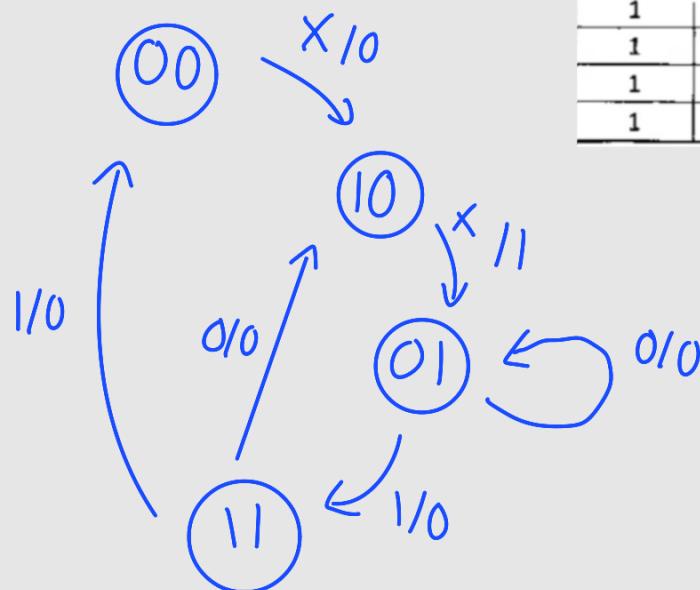

6)

Based on Figure 3, fill up the state table (Table 2) and without excitation table get the SOP (sum of product) for each JK flip flop ($J_a K_a$, $J_b K_b$ and $J_c K_c$) using K-Map to develop a 3-bit (xyz) Gray code counter with the following characteristics:


Leith

- Bila masukan input $y = 1$, mesin membilang menaik dalam kod Gray
When input given $y = 1$, machine count upward in Gray code
- Bila masukan input $y = 0$, mesin membilang menurun dalam kod Gray
When input given $y = 0$, machine count downward in Gray code

*fill up state table

Table 2: State table for 3 bit up/down Gray code counter

Nombor Minterm Minterm Number	Pengawal Controller	Masukan/Input			Keluaran/Output			
		Keadaan Semasa Current State	a	b	c	Keadaan Berikut Next State	a^*	b^*
0	0	000	0	0	0	001	1	0
1	0	001	0	0	1	000	0	0
3	0	010	0	1	1	001	0	0
2	0	011	0	0	1	010	0	1
6	0	100	1	1	0	011	0	1
7	0	101	1	1	1	110	1	1
5	0	110	1	0	1	111	1	1
4	0	111	1	0	0	010	1	0
12	1	000	1	1	0	001	0	0
13	1	001	1	1	0	010	1	0
15	1	010	1	1	1	011	1	0
14	1	011	1	1	0	110	1	1
10	1	100	1	0	0	111	1	0
11	1	101	1	0	1	000	0	1
9	1	110	1	0	0	001	0	1
8	1	111	1	0	0	010	0	1

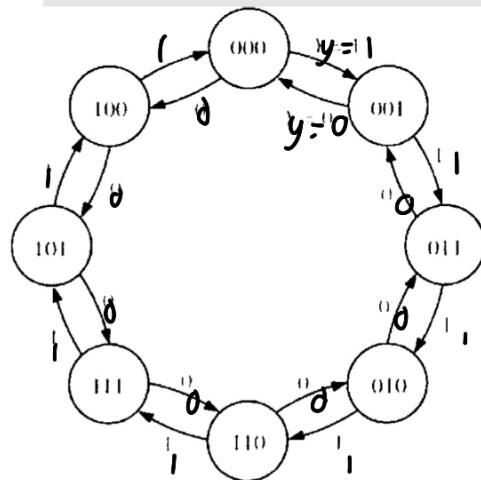


Rajah 3: Gambarajah keadaan untuk pembilang 3 bit kod Gray menaik/menurun.

Figure 3: State diagram for 3 bit up/down Gray code counter.

y_a	b^*	00	01	11	10
00	0	1	0	0	0
01	1	1	1	0	0
11	0	1	1	1	1
10	0	0	0	0	1

(12 markah/marks)

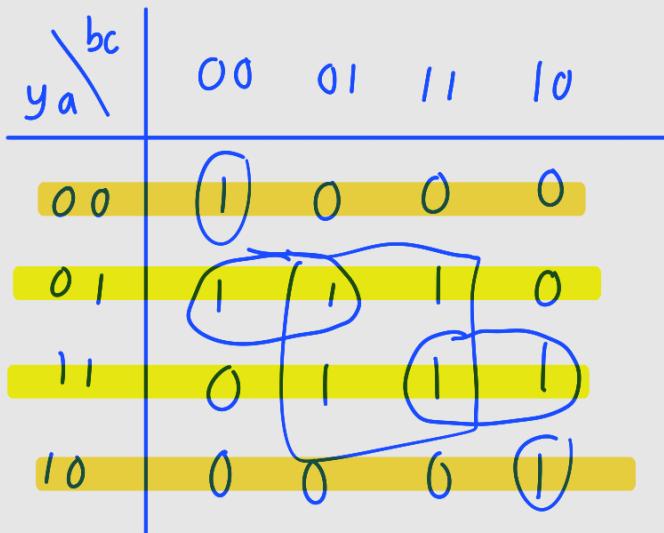

$$J_a = 0 \quad k^1 = 1$$

$$J_A = y' b' c' + y b c'$$

$$K_A' = c + y' b' + y b$$

$$K_A = \frac{c + y' b' + y b}{c + \bar{y} \bar{b} + y b}$$

$$= y \bar{b} \bar{c} + \bar{y} b \bar{c}$$

$$J_A = \bar{y} \bar{b} \bar{c} + y b \bar{c}$$

$$K_A = y \bar{b} \bar{c} + \bar{y} b \bar{c}$$

Leith

$y_a \backslash bc$	00	01	11	10
00	0	0	0	1
01	0	1	1	1
11	0	0	0	1
10	0	1	1	1

$$\begin{aligned}
 J_B &= y'ac + ya'c \\
 K_B &= c' + y'a + ya' \\
 &= \bar{c} \cdot \bar{y}^a \cdot \bar{y}^{a'} \\
 &= c \cdot (\bar{y} + \bar{a}) \cdot (\bar{y} + \bar{a}') \\
 &= (y + \bar{a})(\bar{y}c + ac) \\
 &= y\bar{y}c + yac + \bar{y}\bar{a}c + \bar{a}\bar{a}c \\
 &= yac + \bar{y}\bar{a}c
 \end{aligned}$$

$$J_B = \bar{y}ac + y\bar{a}c$$

$$K_B = yac + \bar{y}\bar{a}c$$

$y_a \backslash bc$	00	01	11	10
00	1	1	1	1
01	1	1	1	1
11	1	1	1	1
10	1	1	1	1

$$\begin{aligned}
 J_c &= y'a'b + y'a'b' + yab + ya'b' \\
 K_c &= \frac{y'a'b + y'a'b' + yab + ya'b'}{y'a'b + y'a'b' + yab + ya'b'} \\
 &= y'a'b + y'a'b' + yab + ya'b'
 \end{aligned}$$

$$J_c = \bar{y}\bar{a}b + \bar{y}a\bar{b} + yab + y\bar{a}\bar{b}$$

$$K_c = y\bar{a}b + ya\bar{b} + \bar{y}ab + \bar{y}\bar{a}\bar{b}$$




Leitn

$$J_A = \bar{y} \bar{b} \bar{c} + y b \bar{c}$$

$$K_A = y \bar{b} \bar{c} + \bar{y} b \bar{c} \quad J_c = \bar{y} \bar{a} b + \bar{y} a \bar{b} + y a b + y \bar{a} \bar{b}$$

$$J_B = \bar{y} a c + y \bar{a} c \quad K_c = y \bar{a} b + y a \bar{b} + \bar{y} a b + \bar{y} \bar{a} \bar{b}$$

$$K_B = y a c + \bar{y} \bar{a} c$$

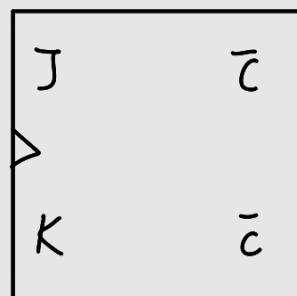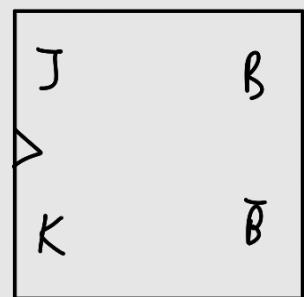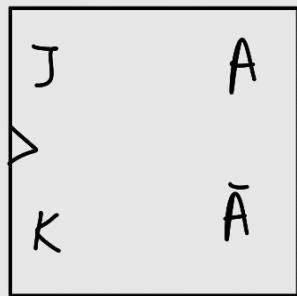

too lazy to draw